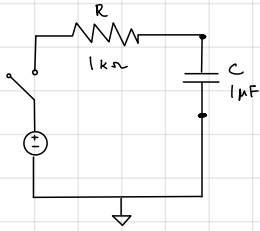


Simple RC Circuit but opening & closing switch every 1.02ms :)




$$\tau = RC = 1000 \Omega \times \frac{1}{1,000,000 \text{ F}}$$

$$\tau = \frac{1}{1000 \text{ s}} = 1 \text{ ms}$$

We use voltage across the capacitor at any time t , for derivation see next page.

$$V_C(t) = \underbrace{V_{\text{source}}}_{0V \sim 5V} + \underbrace{(V_{\text{initial}} - V_{\text{source}})}_{\text{Changes}} e^{-t/\tau}$$
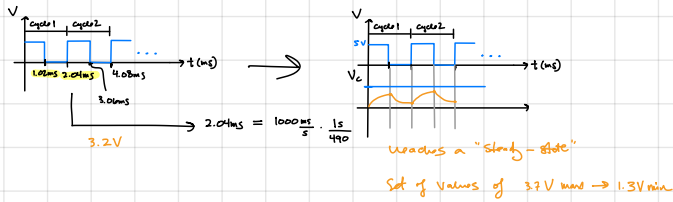
$$f = 490 \text{ Hz} \rightarrow t = \frac{1}{490} = 2.04 \text{ ms}$$



Now, with PWM pin at 50% duty cycle and 490 Hz.

Cycle 1

charging $0 \text{ s} \rightarrow 1.02 \text{ ms} \quad \left| \quad V(1.02 \text{ ms}) = 5V + (0V - 5V) e^{-1.02/0.36059} = \underline{3.14703 \text{ V}}$

discharging $1.02 \text{ ms} \rightarrow 2.04 \text{ ms} \quad \left| \quad V(2.04 \text{ ms}) = 0V + (3.14703 \text{ V} - 0V) \times 0.36059 = \underline{1.15282 \text{ V}} \quad \underline{1.2 \text{ V}}$

Cycle 2

charging $2.04 \text{ ms} \rightarrow 3.06 \text{ ms} \quad \left| \quad V(3.06 \text{ ms}) = 5V + (1.15282 \text{ V} - 5V) \times 0.36059 = \underline{3.6034 \text{ V}} \quad \underline{3.6 \text{ V}}$

discharging $3.06 \text{ ms} \rightarrow 4.08 \text{ ms} \quad \left| \quad V(4.08 \text{ ms}) = 0V + (3.6034 \text{ V} - 0V) \times 0.36059 = \underline{1.30272 \text{ V}} \quad \underline{1.3 \text{ V}}$

Cycle 3

charging $4.08 \text{ ms} \rightarrow 5.10 \text{ ms} \quad \left| \quad V(5.10 \text{ ms}) = 5V + (1.30272 \text{ V} - 5V) \times 0.36059 = \underline{3.66680 \text{ V}} \quad \underline{3.7 \text{ V}}$

discharging $5.10 \text{ ms} \rightarrow 6.12 \text{ ms} \quad \left| \quad V(6.12 \text{ ms}) = 0V + (3.66680 \text{ V} - 0V) \times 0.36059 = \underline{1.33221 \text{ V}} \quad \underline{1.3 \text{ V}}$

Cycle 4

charging $6.12 \text{ ms} \rightarrow 7.14 \text{ ms} \quad \left| \quad V(7.14 \text{ ms}) = 5V + (1.33221 \text{ V} - 5V) \times 0.36059 = \underline{3.67493 \text{ V}} \quad \underline{3.7 \text{ V}}$

discharging $7.14 \text{ ms} \rightarrow 8.16 \text{ ms} \quad \left| \quad V(8.16 \text{ ms}) = 0V + (3.67493 \text{ V} - 0V) \times 0.36059 = \underline{1.32475 \text{ V}} \quad \underline{1.3 \text{ V}}$

Cycle 5

charging $8.16 \text{ ms} \rightarrow 9.18 \text{ ms} \quad \left| \quad V(9.18 \text{ ms}) = 5V + (1.32475 \text{ V} - 5V) \times 0.36059 = \underline{3.67474 \text{ V}} \quad \underline{3.7 \text{ V}}$

discharging $9.18 \text{ ms} \rightarrow 10.20 \text{ ms} \quad \left| \quad V(10.20 \text{ ms}) = 0V + (3.67474 \text{ V} - 0V) \times 0.36059 = \underline{1.32507 \text{ V}} \quad \underline{1.3 \text{ V}}$

Cycle 6


charging $10.20 \text{ ms} \rightarrow 11.22 \text{ ms} \quad \left| \quad V(11.22 \text{ ms}) = 5V + (1.32507 \text{ V} - 5V) \times 0.36059 = \underline{3.67486 \text{ V}} \quad \underline{3.7}$

discharging $11.22 \text{ ms} \rightarrow 12.24 \text{ ms} \quad \left| \quad V(12.24 \text{ ms}) = 0V + (3.67486 \text{ V} - 0V) \times 0.36059 = \underline{1.31512 \text{ V}} \quad \underline{1.3 \text{ V}}$

Cycle 7

charging $12.24 \text{ ms} \rightarrow 13.26 \text{ ms} \quad \left| \quad V(13.26 \text{ ms}) = 5V + (1.31512 \text{ V} - 5V) \times 0.36059 = \underline{3.67499 \text{ V}} \quad \underline{3.7 \text{ V}}$

discharging $13.26 \text{ ms} \rightarrow 14.28 \text{ ms} \quad \left| \quad V(14.28 \text{ ms}) = 0V + (3.67499 \text{ V} - 0V) \times 0.36059 = \underline{1.31512 \text{ V}} \quad \underline{1.3 \text{ V}}$

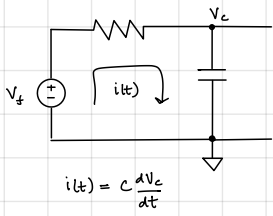

Derivation of Voltage equations

Initial conditions: V_i = initial voltage across capacitor

Start: Kirchhoff's voltage eqn

$$V_f = V_R(t) + V_C(t)$$

$$V_f = i(t)R + V_C(t)$$

Where current through C is $i(t) = C \frac{dV_C(t)}{dt}$

$$V_f = C \frac{dV_C(t)}{dt} R + V_C(t)$$

rearrange

$$\frac{dV_C(t)}{dt} = \frac{V_f - V_C(t)}{RC}$$

Substitute $u(t) = V_f - V_C(t)$

$$-\frac{du(t)}{dt} = \frac{du(t)}{dt}$$

$$-\frac{du(t)}{dt} = \frac{u(t)}{RC}$$

$$\int \frac{du(t)}{u(t)} = -\int \frac{dt}{RC}$$

$$\ln|u(t)| = -\frac{t}{RC} + m$$

$$u(t) = e^{-t/RC + m}$$

$$u(t) = m e^{-t/RC}$$

$$V_f - V_C(t) = m e^{-t/RC}$$

$$V_C(t) = V_f - m e^{-t/RC}$$

$$V_C(0) = V_i = V_f - m \quad \text{where } V_i = \text{initial voltage across capacitor}$$

$$m = V_f - V_i$$

$$V_C(t) = V_f - (V_f - V_i) e^{-t/RC}$$

$$V_C(t) = V_f + (V_i - V_f) e^{-t/RC}$$


$$V_C(t) = V_{\text{source}} + (V_{\text{initial}} - V_{\text{source}}) e^{-t/RC}$$

Voltage Divider

used to lower source voltage


Seen everywhere, are useful circuit snippets, need to be familiar with

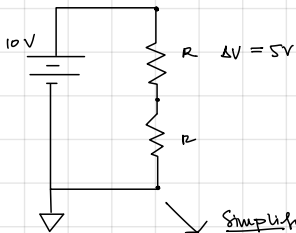Consider series circuit w/ two identical resistors. Ohm's law & Kirchhoff's voltage law tell us:




① Voltage drops over resistor as $V = IR$

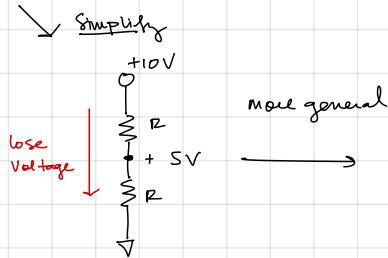② Sum of voltage drops over each R is 10V.



more general

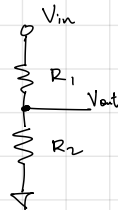

Derivation of Voltage divider eqn.

① total current through circuit

$$V_{in} = I(R_1 + R_2)$$

$$I = \frac{V_{in}}{(R_1 + R_2)}$$

② Voltage across R_2

$$V_{out} = I R_2$$

Subst. in I

$$V_{out} = V_{in} \frac{R_2}{R_1 + R_2}$$

